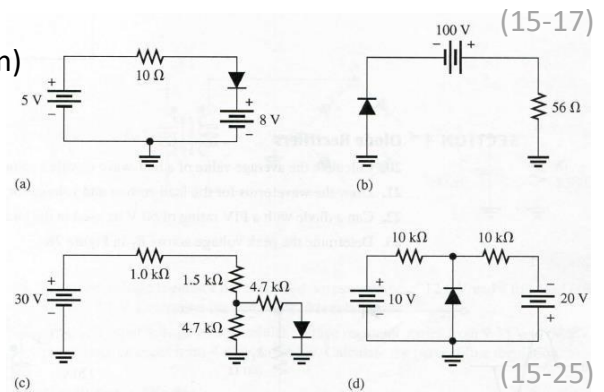


Electronic Circuits Homework 5



1. Determine the voltage across each diode in Figure.

(a) $8 - 5 = 3 \text{ V}$ (b) 0 (c) 0 (d) 10 V (by Superposition)




2. Consider the circuit in Figure.

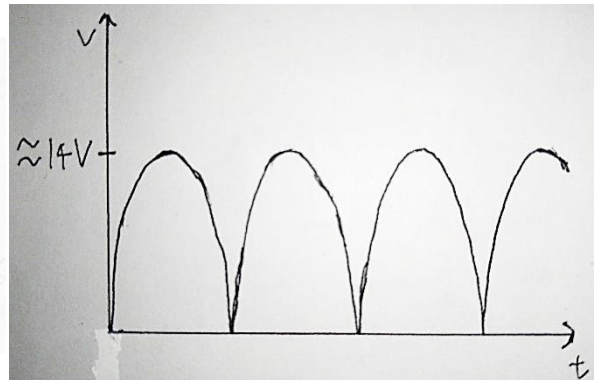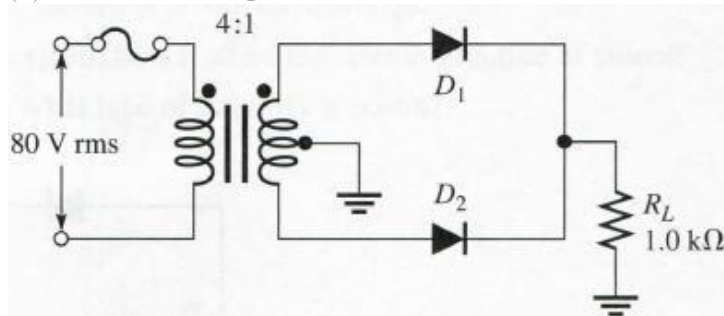(a) What type of circuit is this? **center-tapped full-wave rectifier**
 (b) What is the total peak secondary voltage? $80/0.707/4 \approx 28 \text{ V}$
 (c) Find the peak voltage across each half of the secondary. $\approx 14 \text{ V}$
 (d) Draw the voltage waveform across R_L .





(e) What is the peak current through each diode? $\approx 14/1000 \text{ A} = 14 \text{ mA}$
 (f) What is the PIV for each diode? $\approx 28 \text{ V}$

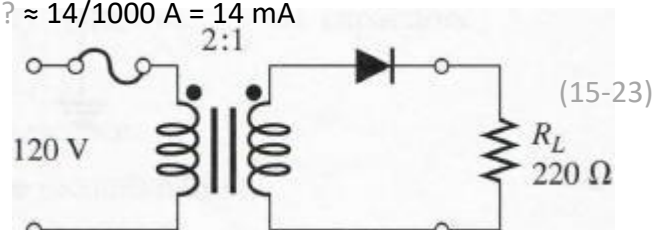3. Determine the peak voltage across R_L in Figure.
 $120/2 - 0.7 \approx 60 \text{ V}$



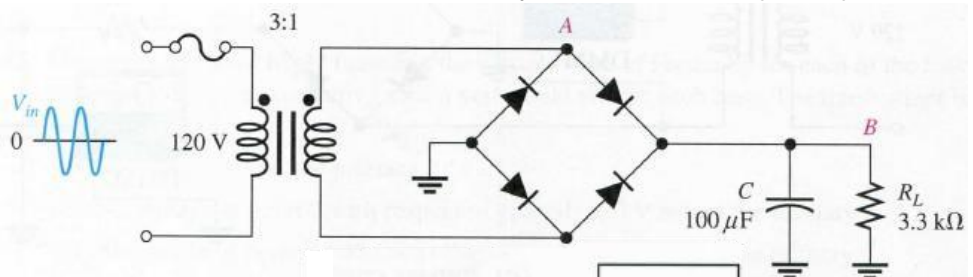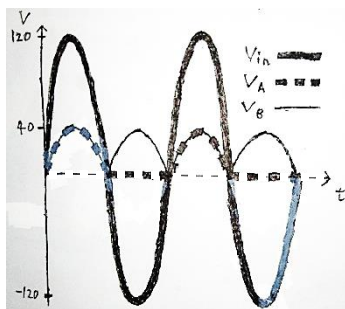4. Refer to Figure and draw the waveforms V_A and V_B with relation to the input waveform. (15-30)



5. Find I_B , I_E , and I_C in Figure given that $\alpha_{DC} = 0.98$ and $\beta_{DC} = 49$.

$$I_E = (2 - 0.7) / 1 = 1.3 \text{ mA}$$

$$I_C = 1.3 \times 0.98 = 1.274 \text{ mA}$$

$$I_B = 1.274 / 49 = 0.026 \text{ mA} = 26 \mu\text{A}$$

6. For the circuit in Figure, find V_B , V_E , I_E , I_C , and V_C .



$$V_B \approx 12 \times (10 / (10 + 22)) = 3.75 \text{ V}$$

$$V_E \approx 3.75 - 0.7 = 3.05 \text{ V}$$

$$I_E \approx 3.05 / 0.68 \approx 4.485 \text{ mA}$$


$$I_C \approx 4.485 \text{ mA}$$
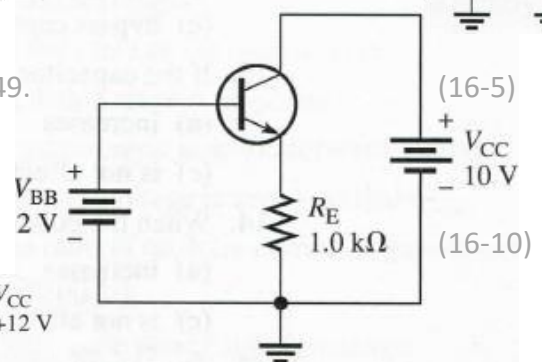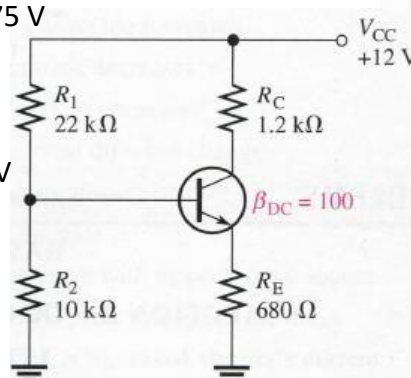
$$V_C \approx 12 - 4.485 \times 1.2 = 6.618 \text{ V}$$



7. Determine the following dc values for the amplifier in Figure:

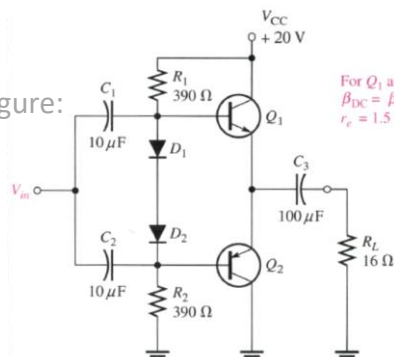
- (a) $V_B \approx 18 \times (12 / (12 + 47)) \approx 3.661 \text{ V}$
 (b) $V_E \approx 3.661 - 0.7 = 2.961 \text{ V}$
 (c) $I_E \approx 2.961 / 1 = 2.961 \text{ mA}$
 (d) $I_C \approx 2.961 \text{ mA}$
 (e) $V_C \approx 18 - 2.961 \times 3.3 = 8.2287 \text{ V}$
 (f) $V_{CE} \approx 8.2287 - 2.961 = 5.2677 \text{ V}$



For Q_1 and Q_2 :
 $\beta_{DC} = \beta_{ac} = 200$
 $r_e = 1.5 \Omega$

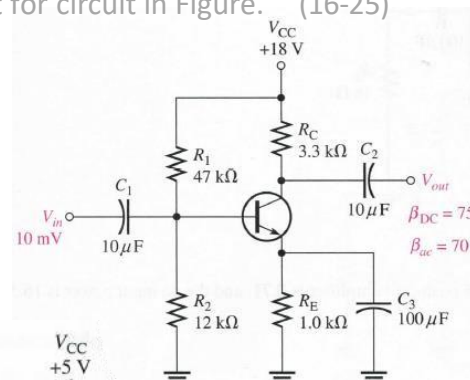8. Determine the maximum peak output voltage and peak load current for circuit in Figure. (16-25)

maximum peak output $\approx 20 / 2 = 10 \text{ V}$
 peak load current $\approx 10 / 16 = 0.625 \text{ A}$



9. Determine $I_{C(sat)}$ for the transistor in Figure.


What is the value of I_B necessary to produce saturation?

What minimum value of V_{IN} is necessary for saturation?

When $V_{IN} = V_{CC} = 5 \text{ V}$:




$$I_{C(sat)} = 5 / (10 \times 100 / (10 + 100)) \times (100 / (100 + 10)) = 0.5 \text{ mA}$$
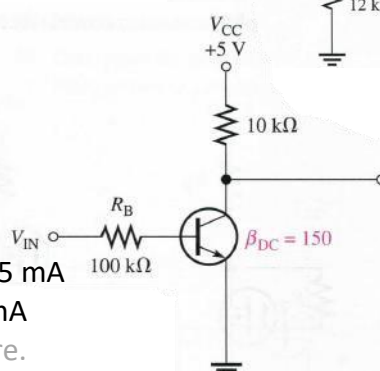
$$I_B = 5 / (10 \times 100 / (10 + 100)) \times (10 / (100 + 10)) = 0.05 \text{ mA}$$






10. Identify the type of input mode for each op-amp in Figure.

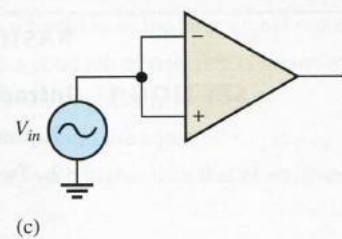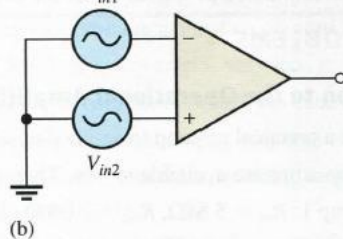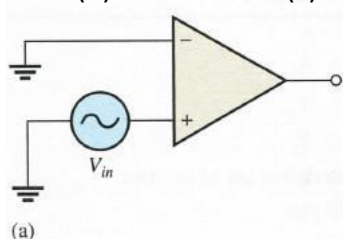(a) single-ended (b) differential (c) common







11. Identify each of the op-amp configurations in Figure.

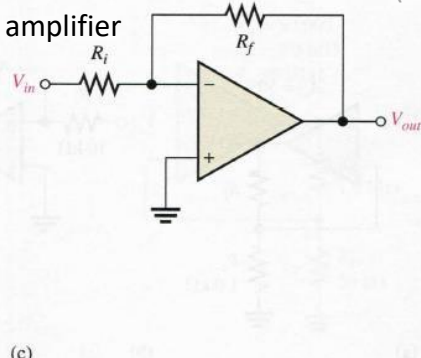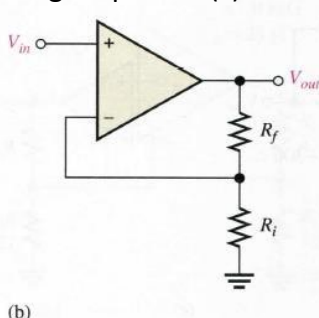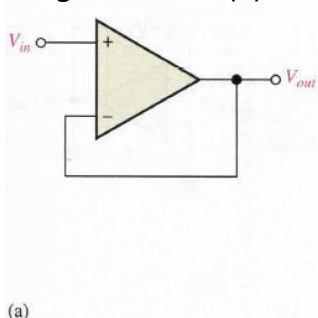(a) voltage-follower (b) noninverting amplifier (c) inverting amplifier



12. Find the gain of each amplifier in Figure.

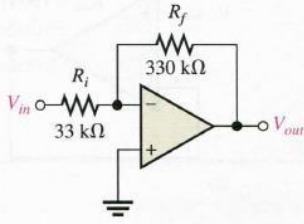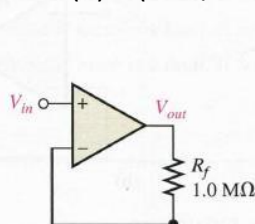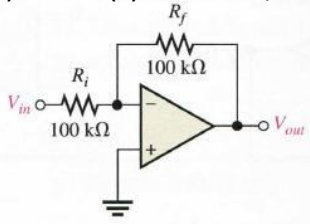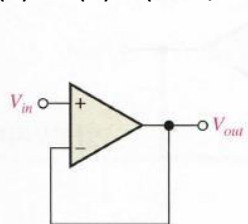
(a) 1 (b) $-(100 / 100) = -1$ (c) $1 + 1000 / 47 \approx 22$ (d) $-(330 / 33) = -10$



13. Determine the output level (maximum positive or maximum negative) for each comparator in Figure.



(a) maximum negative (b) maximum positive (c) maximum negative

(18-1)

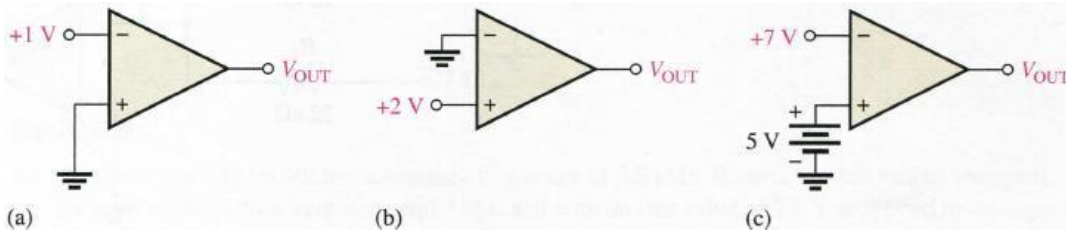

14. Draw the output voltage waveform for each circuit in Figure with respect to the input. Show voltage levels.


(18-3)

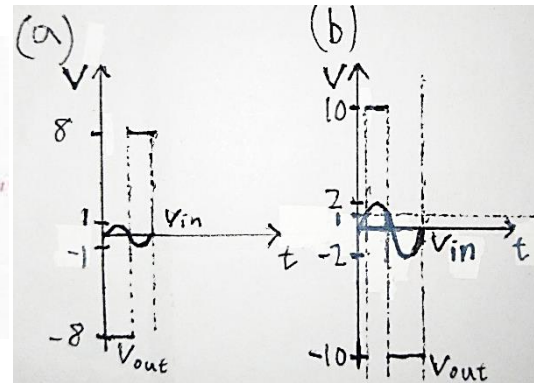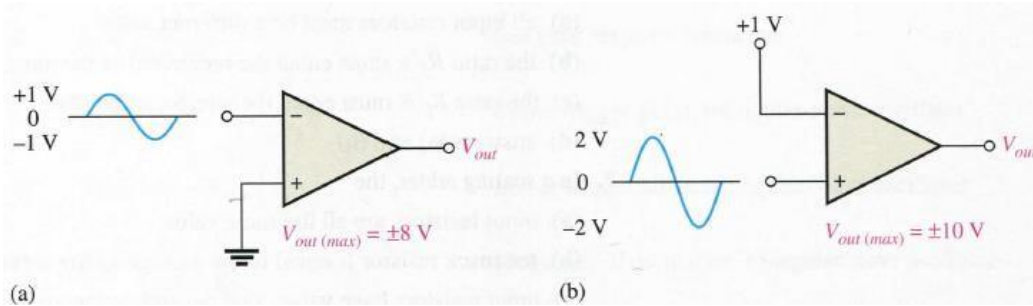

15. Determine the output voltage for each circuit in Figure.

(a) $1 + 1.5 = 2.5 V$ (b) $(-0.1 + 1 + 0.5) \times 22 / 10 = 3.08 V$


(18-4)

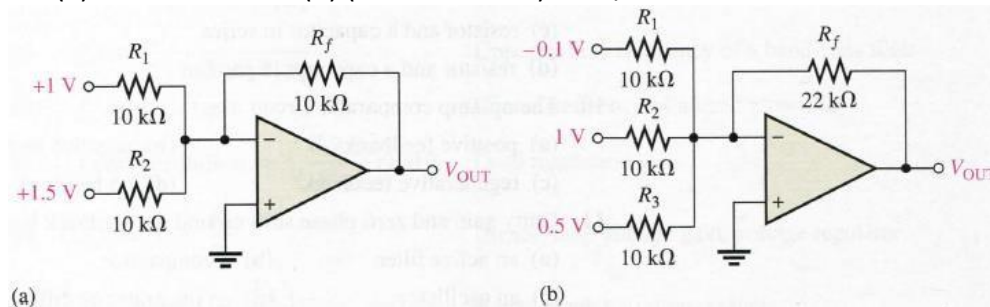

16. Determine the rate of change of the output voltage in response to the step input to the ideal integrator in Figure.

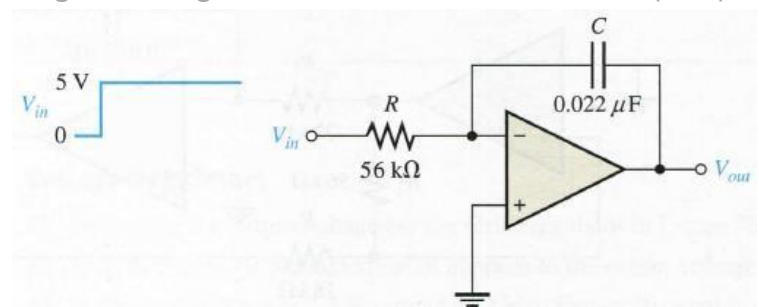(18-9)

$-(5 / 56000 / 0.000000022) \approx -4058 V/s$



17. A triangular waveform is applied to the input of the ideal differentiator in Figure as shown.

Determine what the output should be, and draw its waveform in relation to the input. (18-10)

$-(5 / (0.00001 / 2) \times 10000 \times 0.000000001) = -10 V$

