

Electronic Circuits Homework 4

1. Determine the total inductance of each circuit in Figure 1. (11-12)

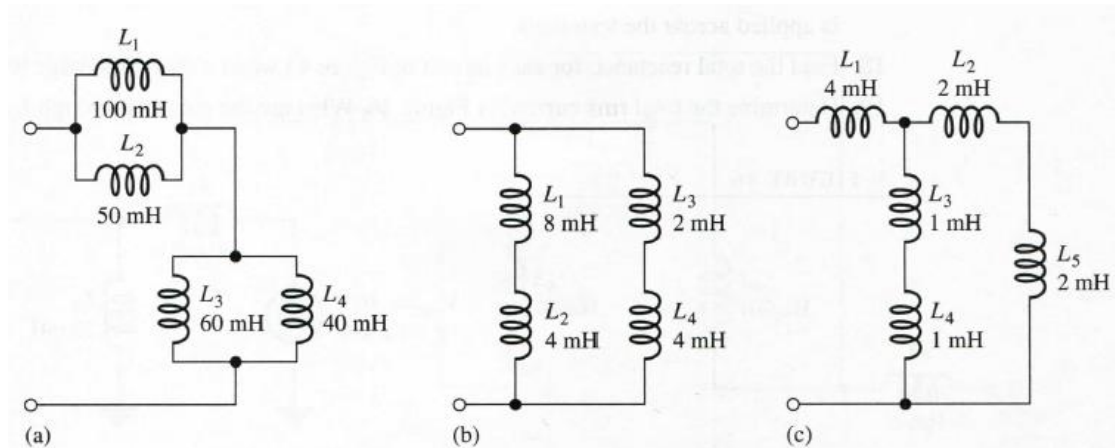


Figure 1

2. Determine the time constant for each of the following series RL combinations:
 (a) $R=100\Omega$, $L=100\mu\text{H}$ (b) $R=4.7\text{k}\Omega$, $L=10\text{mH}$ (c) $R=1.5\text{M}\Omega$, $L=3\text{H}$ (11-13)

3. In the circuit of Figure 2, there is initially no current. Determine the inductor voltage at the following times after the switch is closed:
 (a) $10\mu\text{s}$ (b) $20\mu\text{s}$ (c) $30\mu\text{s}$ (d) $40\mu\text{s}$ (e) $50\mu\text{s}$ (11-15)

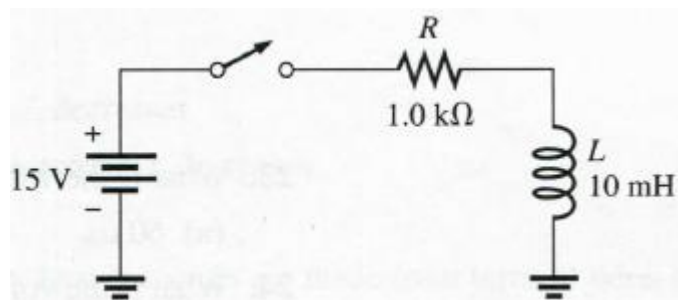


Figure 2

4. Determine the impedance and phase angle in each circuit in figure 3. (12-4)

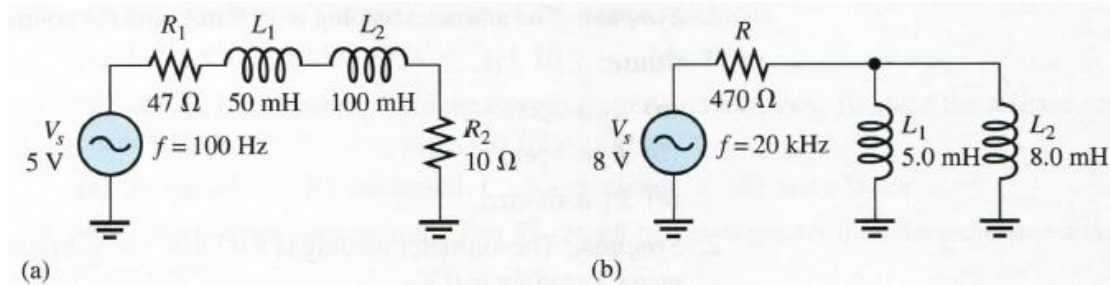


Figure 3

5. Draw the waveforms for V_s , V_R , and V_L in Figure 4. Show the proper phase relationships. (12-13)

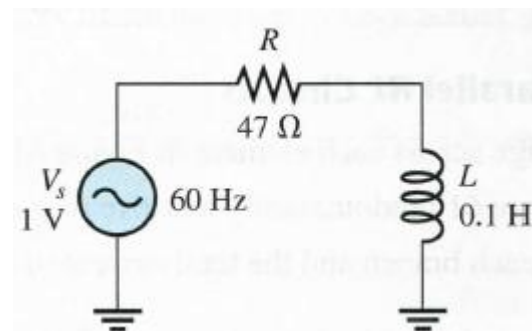


Figure 4

6. Plot the response curve for the circuit in Figure 5. Show the output voltage versus frequency in 1 kHz increments from 0 Hz to 5 kHz. (12-30)

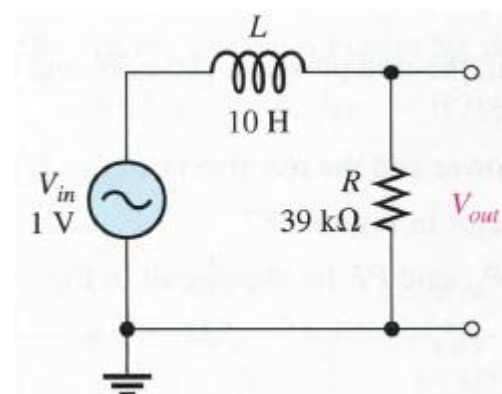


Figure 5

7. A certain series RLC circuit operates at a frequency of 5 kHz and has the following values:
 $R=10\Omega$, $C=0.047\mu\text{F}$, and $L=5\text{mH}$. Determine the impedance and phase angle.
 What is the total reactance? (13-1)
8. For the RLC circuit in Figure 6, determine the resonant frequency and the cutoff frequencies. (13-11)

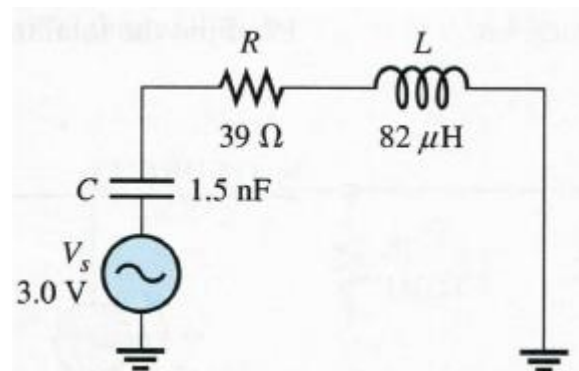


Figure 6

9. Determine f_r and BW for each filter in Figure 7. (13-15)

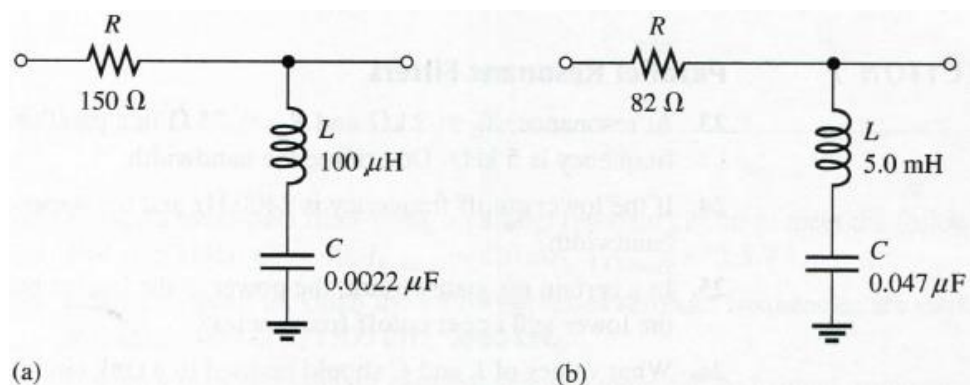


Figure 7

10. Determine the following quantities in Figure 8 :

- (a) secondary voltage
- (b) secondary current
- (c) primary current
- (d) power in the load

(7th14-18)

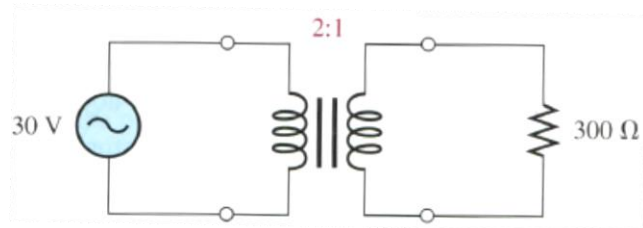


Figure 8

11. In Figure 9, what is the maximum power in watts delivered to the speaker?

(7th14-24)

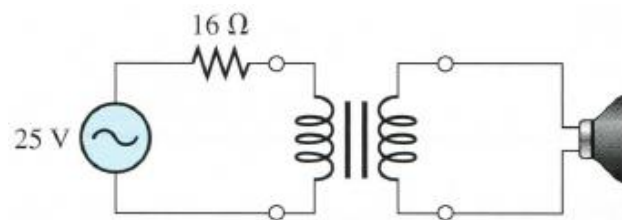


Figure 9

12. Determine the output voltage for the circuit in Figure 10. A single-pulse input is applied as shown.

(14-16)

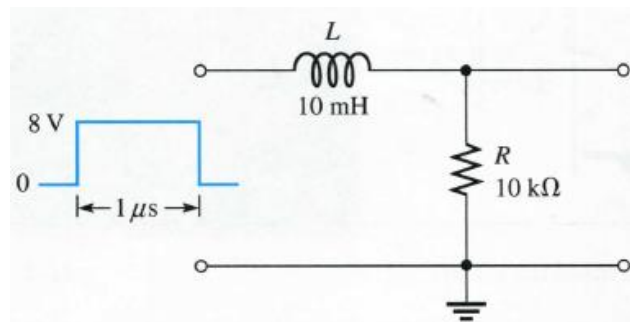


Figure 10

13. (a) What is τ in Figure 11?
(b) Draw the output voltage.

(14-18)

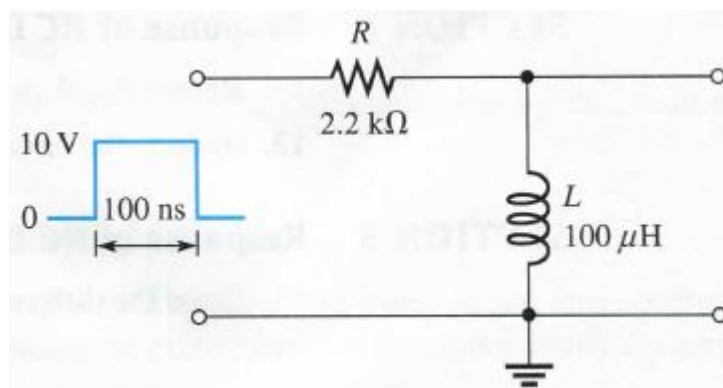


Figure 11