

### Electronic Circuits Homework 3

1. A sine wave goes through 5 cycles in 10  $\mu$ s. What is its period? 2  $\mu$ s (8-3)
2. A sine wave has a peak value of 12 V. Determine the following voltage values: (8-6)
  - (a) rms 8.484 (b) peak-to-peak 24 (c) half-cycle average 7.644
3. A sinusoidal voltage is applied to the resistive circuit in Figure 1. Determine the following: (8-21)
  - (a)  $I_{rms}$  (b)  $I_{avg}$  (c)  $I_p$  (d)  $I_{pp}$  (e)  $i$  at the positive peak

- (a)  $\frac{10}{1000} \times 0.707 = 0.00707 \text{ (A)} = 7.07 \text{ (mA)}$   
 (b)  $\frac{10}{1000} \times 0.637 = 0.00637 \text{ (A)} = 6.37 \text{ (mA)}$   
 (c)  $\frac{10}{1000} = 0.01 \text{ (A)} = 10 \text{ (mA)}$   
 (d)  $\frac{10}{1000} \times 2 = 0.02 \text{ (A)} = 20 \text{ (mA)}$   
 (e)  $= I_p = 10 \text{ (mA)}$



Figure 1

4. Find the half-cycle average value of the voltages across  $R_1$  and  $R_2$  in Figure 2. (8-22)

All values shown are rms.

$$R_1: \frac{120-65}{0.707} \times 0.637 \approx 49.554 \text{ (V)}$$

$$R_2: \frac{65-30}{0.707} \times 0.637 \approx 31.535 \text{ (V)}$$

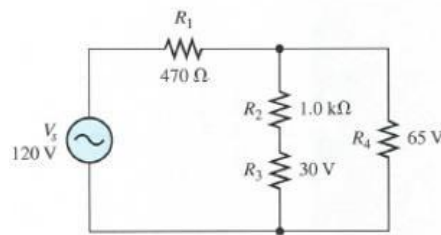


Figure 2

5. (a) Find the capacitance when  $Q = 50 \mu\text{C}$  and  $V = 10 \text{ V}$ . 5  $\mu\text{F}$  (9-1)  
 (b) Find the charge when  $C = 0.001 \mu\text{F}$  and  $V = 1 \text{ kV}$ . 1  $\mu\text{C}$   
 (c) Find the voltage when  $Q = 2 \text{ mC}$  and  $C = 200 \mu\text{F}$ . 10 V

6. What size capacitor is capable of storing 10 mJ of energy with 100V across its plates? (9-5)  
 $\frac{10}{1000} = \frac{1}{2} \times C \times 100^2 \rightarrow C = 0.000002 \text{ (F)} = 2 \text{ (}\mu\text{F)}$

7. Find the total capacitance for each circuit in Figure 3. (9-19)

(a)  $\frac{1}{\frac{1}{1} + \frac{1}{2.2}} = 0.6875 \text{ (}\mu\text{F)}$

(b)  $\frac{1}{\frac{1}{100} + \frac{1}{560} + \frac{1}{390}} \approx 69.687 \text{ (pF)}$

(c)  $\frac{1}{\frac{1}{10} + \frac{1}{4.7} + \frac{1}{47} + \frac{1}{22}} \approx 2.635 \text{ (}\mu\text{F)}$

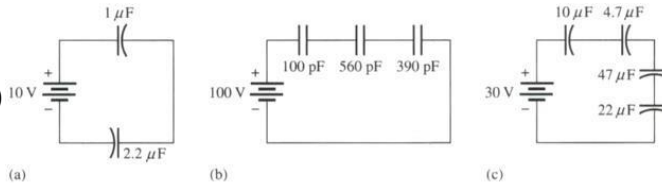


Figure 3

8. The total charge stored by the series capacitors in Figure 4 is 10  $\mu\text{C}$ . Determine the voltage across each of the capacitors. (9-21)

$$C_1 = \frac{10}{4.7} \approx 0.532 \text{ (V)}, C_2 = \frac{10}{1} = 2.5 \text{ (V)}$$

$$C_3 = \frac{10}{2.2} \approx 1.136 \text{ (V)}, C_4 = \frac{10}{10} = 0.25 \text{ (V)}$$

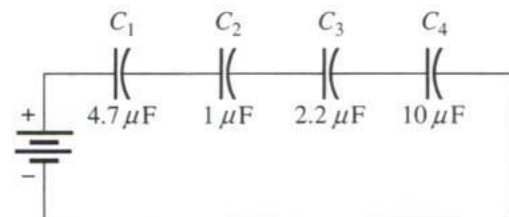


Figure 4

9. Determine  $C_T$  for each circuit in Figure 5. (9-22)

(a)  $47+10+0.001 \times 1000000 = 1057 \text{ (pF)}$

(b)  $0.1+0.01+0.001+10000 \times 0.000001 = 0.121 \text{ (}\mu\text{F)}$

10. Determine the time constant for each of the following series RC combinations: (9-25)

(a)  $R = 100 \Omega$ ,  $C = 1 \mu\text{F}$  0.0001 (s)

(b)  $R = 10 \text{ M}\Omega$ ,  $C = 56 \text{ pF}$  0.00056 (s)

(c)  $R = 4.7 \text{ k}\Omega$ ,  $C = 0.0047 \mu\text{F}$  0.00002209 (s)

(d)  $R = 1.5 \text{ M}\Omega$ ,  $C = 0.01 \mu\text{F}$  0.015 (s)

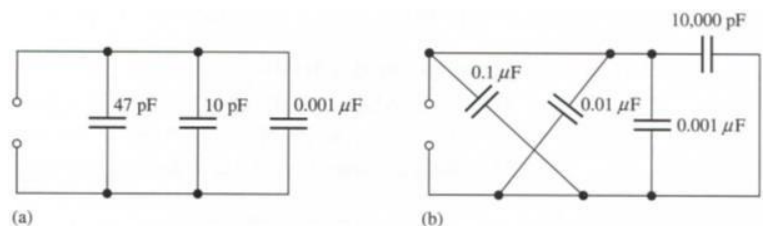


Figure 5

11. In the circuit of Figure 6, the capacitor initially is uncharged. Determine the capacitor voltage at the following times after the switch is closed: (a) 10  $\mu\text{s}$  (b) 20  $\mu\text{s}$  (c) 30  $\mu\text{s}$  (d) 40  $\mu\text{s}$  (e) 50  $\mu\text{s}$  (9-27)

Time constant: 0.00001 (s) = 10 ( $\mu\text{s}$ )

(a)  $15 \times 63\% = 9.45 \text{ (V)}$  (b)  $15 \times 86\% = 12.9 \text{ (V)}$  (c)  $15 \times 95\% = 14.25 \text{ (V)}$

(d)  $15 \times 98\% = 14.7 \text{ (V)}$  (e)  $15 \times 99\% = 14.85 \text{ (V)}$

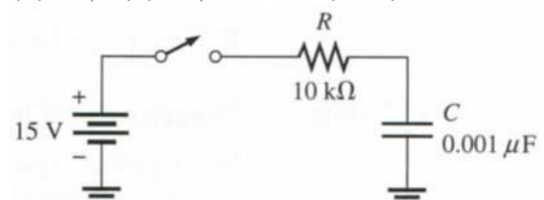


Figure 6

12. Determine  $X_C$  for a  $0.047 \mu\text{F}$  capacitor at each of the following frequencies:

- (a) 10 Hz      (b) 250 Hz      (c) 5 kHz      (d) 100 kHz

(9-31)

$$(a) \frac{1}{2\pi \times 10 \times 0.000000047} \approx 338628 (\Omega) = 338.628 (\text{k}\Omega)$$

$$(b) \frac{1}{2\pi \times 250 \times 0.000000047} \approx 13545 (\Omega) = 13.545 (\text{k}\Omega)$$

$$(c) \frac{1}{2\pi \times 5000 \times 0.000000047} \approx 677.255 (\Omega)$$

$$(d) \frac{1}{2\pi \times 100000 \times 0.000000047} \approx 33.863 (\Omega)$$

13. What is the value of total capacitive reactance in each circuit in Figure 7?

(9-32)

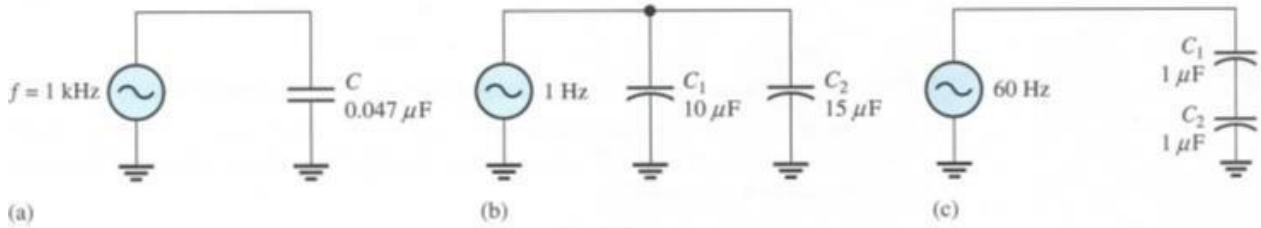


Figure 7

$$(a) \frac{1}{2\pi \times 1000 \times 0.000000047} \approx 3386 (\Omega) = 3.386 (\text{k}\Omega)$$

$$(b) \frac{1}{2\pi \times 1 \times (0.00001 + 0.000015)} \approx 6366 (\Omega) = 6.366 (\text{k}\Omega)$$

$$(c) \frac{1}{2\pi \times 60 \times \frac{1}{\frac{1}{0.000001} + \frac{1}{0.000001}}} \approx 5305 (\Omega) = 5.305 (\text{k}\Omega)$$

14. In each circuit of Figure 7, what frequency is required to produce an  $X_{C(\text{tot})}$  of 100  $\Omega$ ?

(9-34)

An  $X_{C(\text{tot})}$  of 1 k $\Omega$ ?

$$(a) \frac{1}{2\pi \times f \times 0.000000047} = 100 (\Omega) \rightarrow f = \frac{1}{2\pi \times 0.000000047 \times 100} \approx 33862 (\text{Hz}) = 33.862 (\text{kHz})$$

$$\frac{1}{2\pi \times f \times 0.000000047} = 1000 (\Omega) \rightarrow f \approx \frac{33862}{10} (\text{Hz}) \approx 3.386 (\text{kHz})$$

$$(b) \frac{1}{2\pi \times f \times (0.00001 + 0.000015)} = 100 (\Omega) \rightarrow f = \frac{1}{2\pi \times (0.00001 + 0.000015) \times 100} \approx 63.66 (\text{Hz})$$

$$\text{For 1 k}\Omega, f \approx \frac{63.66}{10} = 6.366 (\text{Hz})$$

$$(c) \frac{1}{2\pi \times f \times \frac{1}{2 \times \frac{1}{0.000001}}} = 100 (\Omega) \rightarrow f = \frac{1}{2\pi \times \frac{1}{2 \times \frac{1}{0.000001}} \times 100} \approx 3183 (\text{Hz}) = 3.183 (\text{kHz})$$

$$\text{For 1 k}\Omega, f \approx \frac{3183}{10} = 318.3 (\text{Hz})$$

15. Determine the impedance and the phase angle in each circuit in Figure 8. (10-4)

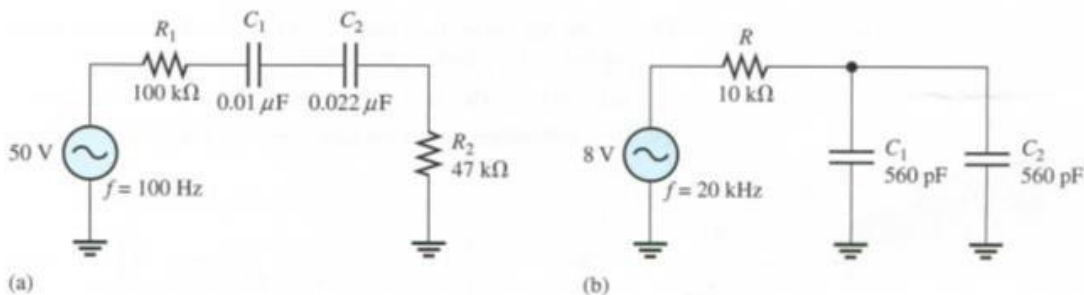


Figure 8

$$(a) X_{C(\text{tot})} = \frac{1}{2\pi \times 100 \times \frac{1}{\frac{1}{0.00000001} + \frac{1}{0.000000022}}} \approx 231498 (\Omega) = 231.498 (\text{k}\Omega)$$

$$\text{value: } \sqrt{(100 + 47)^2 + (X_{C(\text{tot})})^2} \approx 274.227 (\text{k}\Omega)$$

$$\text{angle: } \tan^{-1} \frac{X_{C(\text{tot})}}{100 + 47} \approx 1.0050 (\text{rad})$$

$$(b) X_{C(\text{tot})} = \frac{1}{2\pi \times 20000 \times (2 \times 0.00000000056)} \approx 7105 (\Omega) = 7.105 (\text{k}\Omega)$$

$$\text{value: } \sqrt{10^2 + (X_{C(\text{tot})})^2} \approx 12.267 (\text{k}\Omega)$$

$$\text{angle: } \tan^{-1} \frac{X_{C(\text{tot})}}{10} \approx 0.6177 (\text{rad})$$

16. For the circuit of Figure 9, determine the impedance for each of the following frequencies: (10-5)  
 (a) 100 Hz (b) 500 Hz (c) 1.0 kHz (d) 2.5 kHz

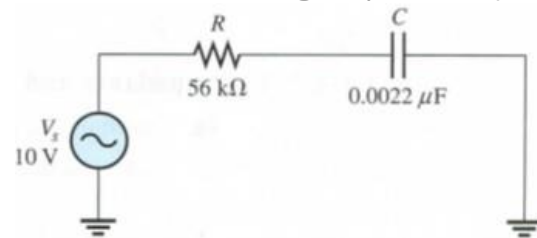


Figure 9

(a) value:  $\sqrt{56000^2 + \left(\frac{1}{2\pi \times 100 \times 0.0000000022}\right)^2} \approx 725595 \text{ } (\Omega) = 725.595 \text{ (k}\Omega\text{)}$   
 angle:  $\tan^{-1} \left( \frac{\frac{1}{2\pi \times 100 \times 0.0000000022}}{56000} \right) \approx 1.4935 \text{ (rad)}$

(b) value:  $\sqrt{56000^2 + \left(\frac{1}{2\pi \times 500 \times 0.0000000022}\right)^2} \approx 155145 \text{ } (\Omega) = 155.145 \text{ (k}\Omega\text{)}$   
 angle:  $\tan^{-1} \left( \frac{\frac{1}{2\pi \times 500 \times 0.0000000022}}{56000} \right) \approx 1.2015 \text{ (rad)}$

(c) value:  $\sqrt{56000^2 + \left(\frac{1}{2\pi \times 1000 \times 0.0000000022}\right)^2} \approx 91485 \text{ } (\Omega) = 91.485 \text{ (k}\Omega\text{)}$   
 angle:  $\tan^{-1} \left( \frac{\frac{1}{2\pi \times 1000 \times 0.0000000022}}{56000} \right) \approx 0.9121 \text{ (rad)}$

(d) value:  $\sqrt{56000^2 + \left(\frac{1}{2\pi \times 2500 \times 0.0000000022}\right)^2} \approx 63035 \text{ } (\Omega) = 63.035 \text{ (k}\Omega\text{)}$   
 angle:  $\tan^{-1} \left( \frac{\frac{1}{2\pi \times 2500 \times 0.0000000022}}{56000} \right) \approx 0.4769 \text{ (rad)}$

17. Determine the impedance and the phase angle in Figure 10. (10-15)

value:  $\frac{1}{\sqrt{\left(\frac{1}{750}\right)^2 + (2\pi \times 2000 \times 0.000000022)^2}} \approx 325.804 \text{ } (\Omega)$

angle:  $\tan^{-1}(2\pi \times 2000 \times 0.000000022 \times 750) \approx 1.1214 \text{ (rad)}$

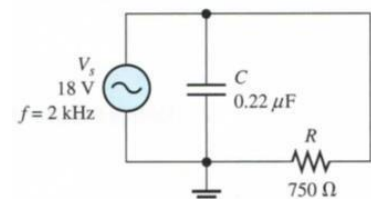


Figure 10

18. For the parallel circuit in Figure 11, find each branch current and the total current.

What is the phase angle between the source voltage and the total current?

(10-19)

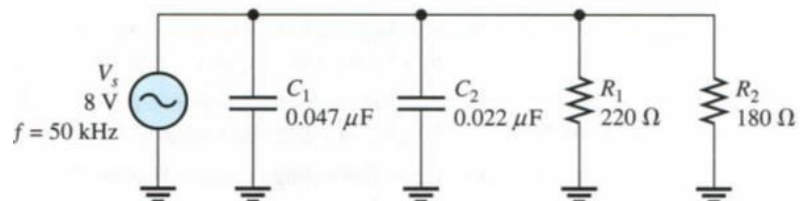


Figure 11

First solve the admittance diagram:

$$G = \frac{1}{220+180} = 0.0025 \text{ (S)}$$

$$B_c = 2\pi \times 50000 \times (0.000000047 + 0.000000022) \approx 0.0217 \text{ (S)}$$

$$Y = \sqrt{(0.0025)^2 + (0.0217)^2} \approx 0.0218 \text{ (S)}$$

$$\angle: \tan^{-1}(B_c \times (220 + 180)) \approx 1.4560 \text{ (rad)}$$

Then multiply by 8 V to get the current phasor diagram:

$$I_R = 0.02 \text{ (A)}, I_C \approx 0.1736 \text{ (A)}$$

$$I_S \approx 0.1744 \text{ (A)}, \angle: \approx 1.4560 \text{ (rad)}$$

Note that current divide among capacitors in parallel are directly proportional to their capacitances.

We apply this rule and the current divider rule with  $I_C$  and  $I_R$  to capacitors and resistors, respectively,

obtaining all branch current:  $I_{C1} \approx 0.1182 \text{ (A)}, I_{C2} \approx 0.0554 \text{ (A)}, I_{R1} = 0.009 \text{ (A)}, I_{R2} = 0.011 \text{ (A)}$

Also remember that all "I-s" above stands for phasor lengths and  $I_S$  represents the phasor of total current.

Since that in a parallel RC circuit, the current through resistor(s) and the source voltage are in phase.

phase angle between source voltage and total current

→ phase angle between source voltage and total current

→ phase angle between  $I_S$  and  $I_R \approx 1.4560 \text{ (rad)}$

19. Determine the voltages across each element in Figure 12. Find the phase angle of the circuit. (10-23)

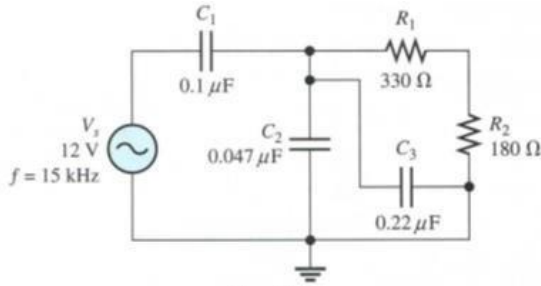


Figure 12

$$Z_{R1,R2,C2,C3} = \frac{1}{\sqrt{\left(\frac{1}{330+180}\right)^2 + (2\pi \times 15000 \times (0.000000047 + 0.00000022))^2}} \approx 39.619 (\Omega)$$

$$\angle_{R1,R2,C2,C3}: \tan^{-1}(2\pi \times 15000 \times (0.000000047 + 0.00000022) \times (330 + 180)) \approx 1.4930 (\text{rad})$$

Convert to equivalent series RC circuit:

$$R_{eq} \approx 39.619 \cos 1.4930 \approx 3.0791 (\Omega)$$

$$X_{C(eq)} \approx 39.619 \sin 1.4930 \approx 39.4992 (\Omega)$$

$$X_{C1} = \frac{1}{2\pi \times 15000 \times 0.0000001} \approx 106.1033 (\Omega)$$

Apply voltage divider rule to  $C_1$ ,  $R_{eq}$ , and  $C_{eq}$  to obtain  $V_{C1} \approx 8.56 \times \sin 30000\pi t$

So  $V_{C2} = V_{C3} \approx 3.44 \times \sin 30000\pi t$ ,  $V_{R1} \approx 2.23 \times \sin 30000\pi t$ ,  $V_{R2} \approx 1.21 \times \sin 30000\pi t$

Also we find the phase angle with the equivalent series RC circuit:

$$R_{tot} = R_{eq} \approx 3.0791 (\Omega)$$

$$X_{C(tot)} = X_{C(eq)} + X_{C1} \approx 145.6025 (\Omega)$$

$$\angle_{tot}: \tan^{-1}\left(\frac{X_{C(tot)}}{R_{tot}}\right) \approx 1.5497 (\text{rad})$$

20. Plot the frequency response curve for the circuit in Figure 13 for a frequency range of 0 Hz to 10 kHz in 1 kHz increments. (10-32)

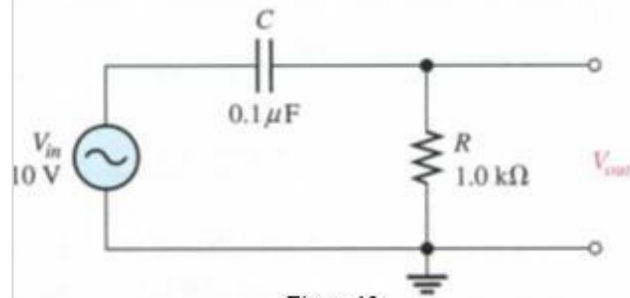
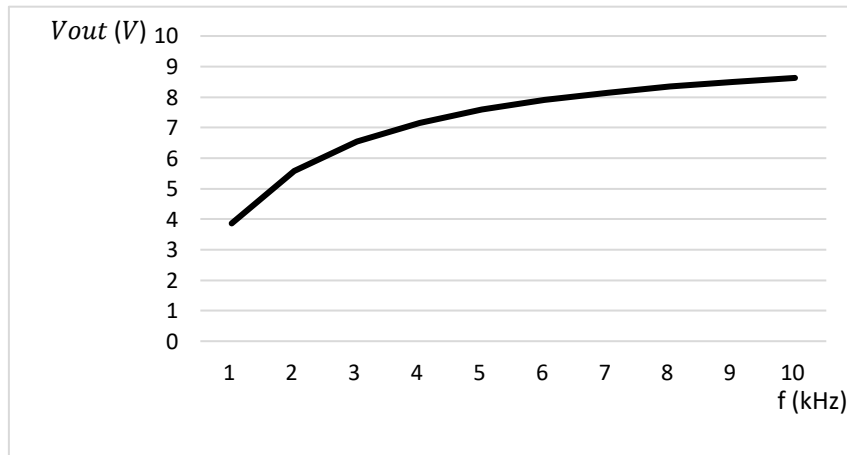


Figure 13