

Electronic Circuits Homework 4


1. Determine the total inductance of each circuit in Figure.

(11-12)

$$(a) \frac{100 \times 50}{100 + 50} + \frac{60 \times 40}{60 + 40} \approx 57(mH)$$

$$(b) \frac{(8+4) \times (2+4)}{(8+4) + (2+4)} = 4(mH)$$
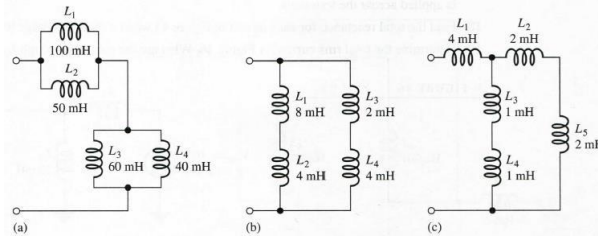
$$(c) \frac{(1+1) \times (2+2)}{(1+1) + (2+2)} + 4 \approx 0.057(H) \approx 5(mH)$$



2. Determine the time constant for each of the following series RL combinations:

(11-13)

(a) $R=100\Omega$, $L=100\mu H$ (b) $R=4.7k\Omega$, $L=10mH$ (c) $R=1.5M\Omega$, $L=3H$

$$1(\mu S)$$

$$\approx 2(\mu S)$$

$$2(\mu S)$$

3. In the circuit of Figure, there is initially no current. Determine the inductor voltage at the following times after the switch is closed: (a) $10\mu s$ (b) $20\mu s$ (c) $30\mu s$ (d) $40\mu s$ (e) $50\mu s$

(11-15)

$$\text{time constant: } \frac{0.01}{1000} = 10(\mu S)$$


$$(a) 15 \times 37\% = 5.55(V)$$

$$(b) 15 \times 14\% = 2.1(V)$$

$$(c) 15 \times 5\% = 0.75(V)$$



$$(d) 15 \times 2\% = 0.3(V)$$

$$(e) 15 \times 1\% = 0.15(V)$$

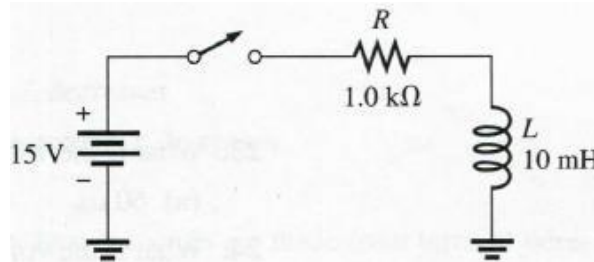

4. Determine the impedance and phase angle in each circuit in Figure.

(12-4)

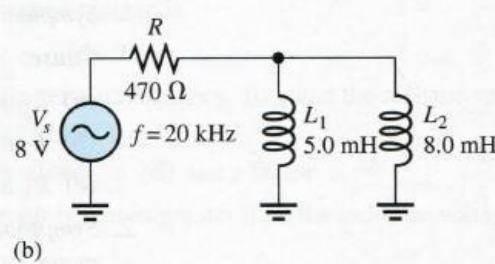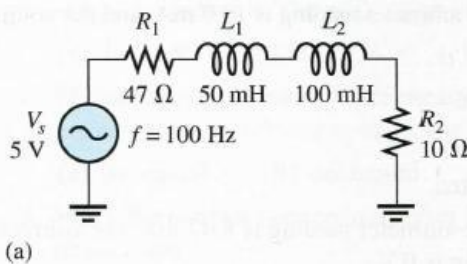

$$(a) X_L = 2\pi \times 100 \times (0.05 + 0.1) \approx 94.25(\Omega)$$

$$Z = \sqrt{X_L^2 + (47 + 10)^2} \approx 110(\Omega)$$

$$\angle: \tan^{-1} \frac{X_L}{47+10} \approx \tan^{-1} 1.65$$

$$(b) X_L = 2\pi \times 20000 \times \frac{0.005 \times 0.008}{0.005 + 0.008} \approx 386.66(\Omega)$$

$$Z = \sqrt{X_L^2 + 470^2} \approx 609(\Omega)$$

$$\angle: \tan^{-1} \frac{X_L}{470} \approx \tan^{-1} 0.82$$

5. Draw the waveforms for V_s , V_R and V_L in Figure. Show the proper phase relationships

(12-13)



$$X_L = 2\pi \times 60 \times 0.1 \approx 37.70(\Omega)$$

$$Z = \sqrt{X_L^2 + 47^2} \approx 60.25(\Omega)$$

$$\angle: \tan^{-1} \frac{X_L}{47} \approx \tan^{-1} 0.80 \approx 38.66^\circ$$



$$V_{R\text{-peak}} = \sqrt{1^2 \times \frac{47}{X_L + 47}} \approx 0.74(V)$$
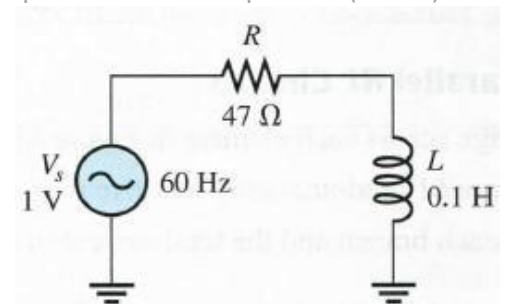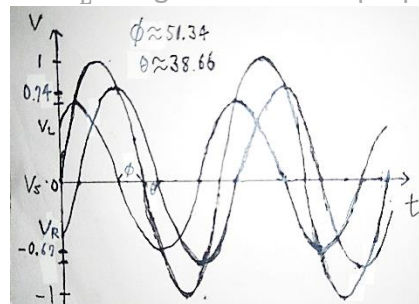
$$V_{L\text{-peak}} = \sqrt{1^2 \times \frac{X_L}{X_L + 47}} \approx 0.67(V)$$



6. Plot the response curve for the circuit in Figure. Show the output voltage versus frequency in 1 kHz increments from 0 Hz to 5 kHz.

(12-30)

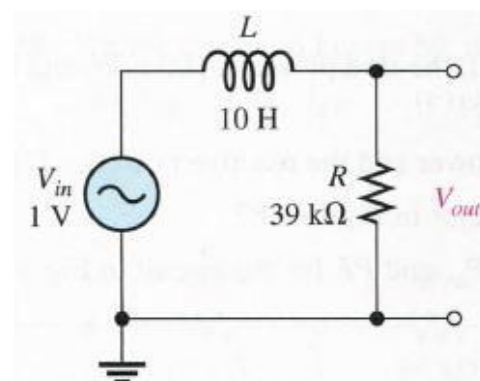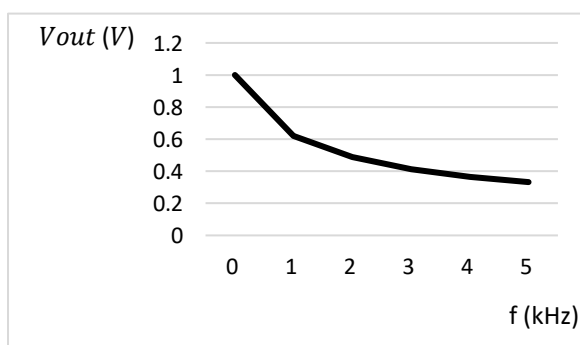

7. A certain series RLC circuit operates at a frequency of 5 kHz and has the following values: $R=10\Omega$, $C=0.047\mu\text{F}$, and $L=5\text{mH}$. Determine the impedance and phase angle. What is the total reactance?

$$X_C = \frac{1}{2\pi \times 5000 \times 0.000000047} \approx 677(\Omega), X_L = 2\pi \times 5000 \times 0.005 \approx 157(\Omega) \quad (13-1)$$

$$\text{Total Reactance } X_{\text{tot}} \approx 677 - 157 = 520(\Omega)$$

$$Z_{\text{tot}} = \sqrt{X_{\text{tot}}^2 + 10^2} \approx 520(\Omega), \angle: \tan^{-1} \frac{X_{\text{tot}}}{10} = \tan^{-1} 52$$

8. For the RLC circuit in Figure, determine the resonant frequency and the cutoff frequencies. (13-11)

$$f_r = \frac{1}{2\pi \times \sqrt{0.000082 \times 0.0000000015}} \approx 453803(\text{Hz})$$

$$f_c = \frac{\pm(39 \times 0.0000000015) + \sqrt{(39 \times 0.0000000015)^2 + 4 \times 0.000082 \times 0.0000000015}}{4\pi \times 0.000082 \times 0.0000000015}$$

$$\rightarrow f_1 \approx 417531(\text{Hz}), f_2 \approx 493227(\text{Hz})$$


9. Determine f_r and BW for each filter in Figure 7.

$$(a) f_r = \frac{1}{2\pi \times \sqrt{0.0001 \times 0.0000000022}} \approx 339319(\text{Hz})$$


$$BW = \frac{150}{2\pi \times 0.0001} \approx 238732(\text{Hz})$$

$$(b) f_r = \frac{1}{2\pi \times \sqrt{0.005 \times 0.0000000047}} \approx 10382(\text{Hz})$$
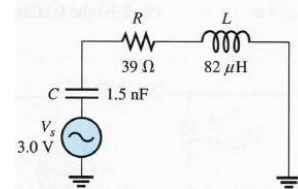
$$BW = \frac{82}{2\pi \times 0.005} \approx 2610(\text{Hz})$$



(13-15)

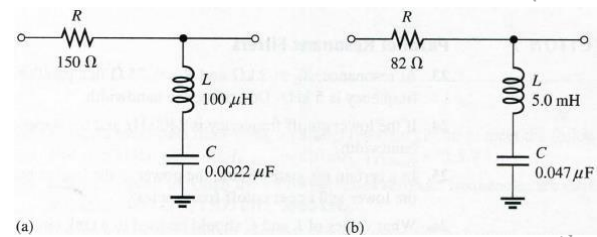


(a)

(b)

(7th 14-18)

10. Determine the following quantities in Figure:

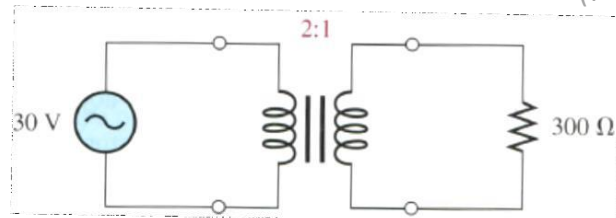
- (a) secondary voltage 15 V
- (b) secondary current 50 mA
- (c) primary current 25 mA
- (d) power in the load 0.75 W



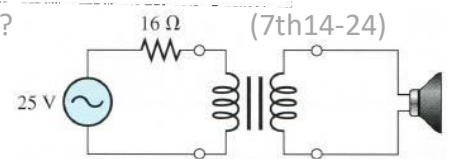11. In Figure, what is the maximum power in watts delivered to the speaker?



When Impedance matched, same with power consumed by the resistor:

$$\frac{25^2}{16+16} \approx 19.53(\text{W})$$



(7th 14-24)

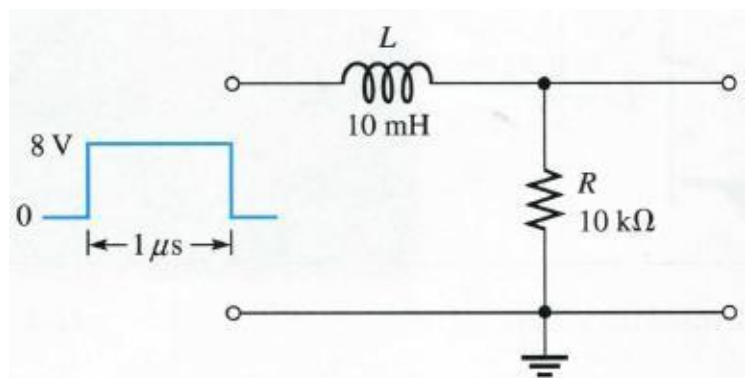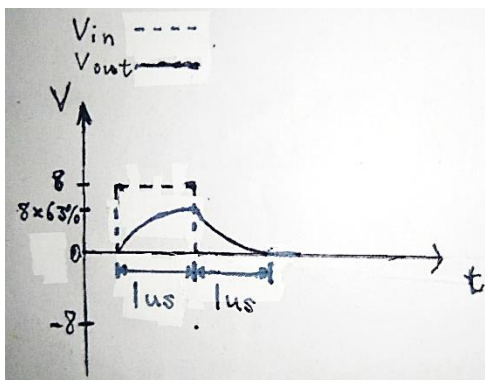12. Determine the output voltage for the circuit in Figure. A single-pulse input is applied as shown. (14-16)



13. (a) What is τ in Figure? $\approx 45 \text{ nS}$

- (b) Draw the output voltage.

(14-18)

